


# Introduction

IN this chapter we describe power electronics and present a brief introduction to semiconductor switching devices and magnetic components. An introduction to these circuit elements is necessary because we utilize them in Part I, although we do not discuss them in detail until Part III. We also introduce nomenclature that we use throughout the book.

## 1.1 POWER ELECTRONIC CIRCUITS

The dominant application of electronics today is to process information. The computer industry is the biggest user of semiconductor devices, and consumer electronics, including cameras, is second. While all these applications require power (from a wall plug or a battery), their primary function is to process information; to take the digital optical signal produced by a compact disk and transform it into an analog audio signal, for instance. Power electronic circuits are principally concerned with processing energy. They convert electrical energy from the form supplied by a source to the form required by a load. For example, the part of a computer that takes the ac mains voltage and changes it to the 5-V dc required by the logic chips is a power electronic circuit (often abbreviated as *power circuit*). In many applications the conversion process concludes with mechanical motion. In these cases the power circuit converts electric energy to the form required by the electromechanical transducer, such as a dc motor.

Efficiency is an important concern in any energy processing system, for the difference between the energy into the system and the energy out is usually converted to heat. Although the cost of energy is sometimes a consideration, the most unpleasant consequence of generating heat is that it must be removed from the system. This consideration alone dictates the size of power electronic apparatus. Therefore a power circuit must be designed to operate as efficiently as possible. The efficiency of very large systems exceeds 99%. High efficiency is achieved by using

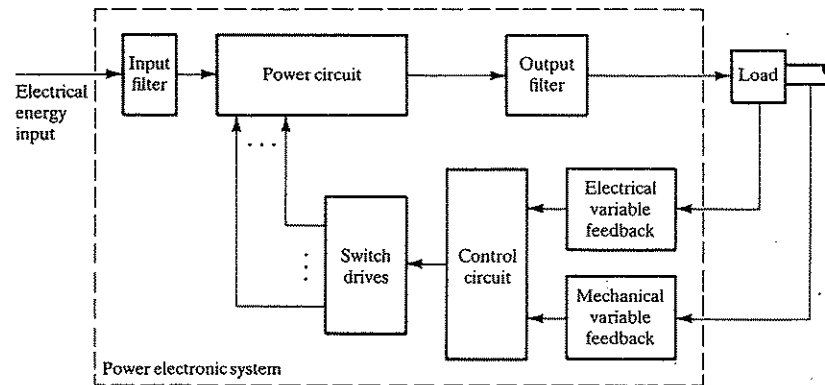

**Figure 1.1** A block diagram of a typical power electronic system.


the power semiconductors as switches (where their voltage is nearly zero when they are on, and their current is nearly zero when they are off) to minimize their dissipation.<sup>†</sup> The only other components in the basic power circuit are inductors and capacitors, so the ideal power circuit is lossless.

A power electronic system consists of much more than a power circuit. The block diagram of a typical system is shown in Fig. 1.1. Switching creates waveforms with harmonics that may be undesirable because they interfere with proper operation of the load or other equipment, so filters are often employed at the inputs and outputs of the power circuit. The system load, which may be electrical or electromechanical, is controlled via the feedback of electrical and/or electromechanical variables to a control circuit. This control circuit processes the feedback signals and drives the switches in the power circuit according to the demands of these signals. The system also includes mechanical elements, such as heat sinks and structures to support the physically large components of the power circuit.

## 1.2 POWER SEMICONDUCTOR SWITCHES

The basic semiconductor devices used as switches in power electronic circuits are the bipolar and Schottky diodes, the bipolar junction transistor (BJT), the metal-oxide-semiconductor field-effect transistor (MOSFET), and a class of latching bipolar devices known as thyristors, the most common of which is the silicon controlled rectifier (SCR). Their circuit symbols and operating regions in the  $v$ - $i$  plane are shown in Fig. 1.2. We discuss these and other hybrid devices in detail in Part III.

<sup>†</sup>Exceptions, such as linear voltage regulators, are so few that we do not consider them explicitly in this book.

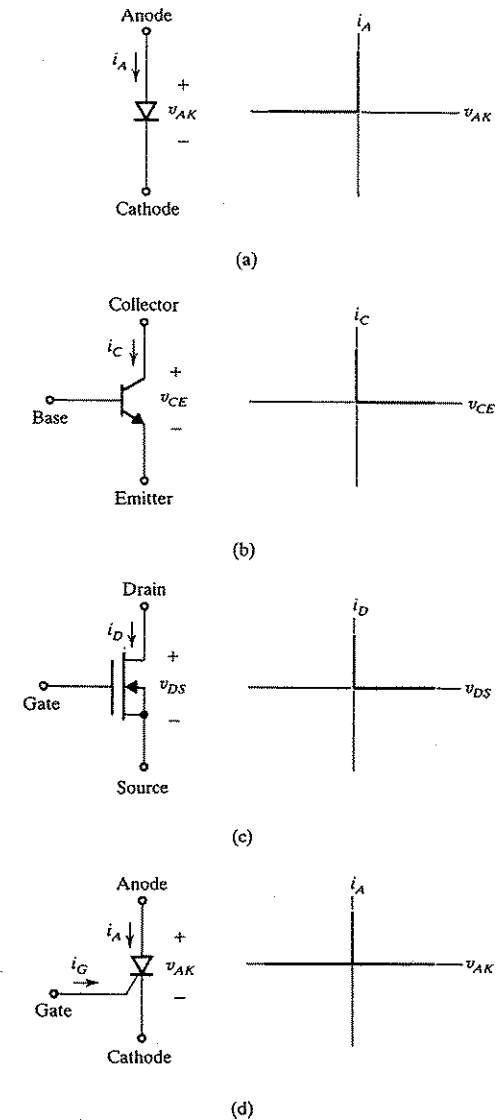

**Figure 1.2** Circuit symbols and operating regions for semiconductor devices used as switches in power electronic circuits: (a) the diode; (b) the (nnp) bipolar junction transistor (BJT); (c) the (n-channel) power metal-oxide-semiconductor field-effect transistor (MOSFET); (d) the silicon controlled rectifier (SCR).

What follows is a brief description of the salient operating characteristics of each device shown in Fig. 1.2. This information allows us to present the basic operation of power electronic circuits without first considering Part III.

### 1.2.1 The Diode

The diode, whose symbol and variable definitions are shown in Fig. 1.2(a), is an uncontrollable semiconductor switch. It is uncontrollable because whether it is on or off is determined by the voltages and currents in the network, not by any action we can take. When on, its anode current,  $i_A$ , is positive. When off, its anode-cathode voltage,  $v_{AK}$ , is negative.<sup>†</sup> The diode switches in response to the behavior of its terminal variables. If it is off and the circuit causes  $v_{AK}$  to try to go positive, the diode will turn on. If on, the diode will turn off if the circuit tries to force  $i_A$  to go negative.

### 1.2.2 The Transistor

Transistors, whether of the bipolar or MOS type, are fully controllable switches. They possess a third terminal (the *base* terminal for the BJT and the *gate* terminal for the MOSFET) from which we can turn the device on and off. The symbols and terminal variables for the npn BJT and n-channel power MOSFET are shown in Fig. 1.2(b) and (c). Both of these devices can carry current in only one direction, and for the npn BJT and n-channel MOSFET shown in the figure, these directions are  $i_C > 0$  and  $i_D > 0$ , respectively. When off, they can support only one polarity of voltage, which, for the transistors shown, are  $v_{CE} > 0$  and  $v_{DS} > 0$ . These voltage and current polarities are reversed for the pnp BJT and the p-channel MOSFET. But, for reasons discussed in Part III, npn and n-channel devices are the most commonly used types of power transistors.

### 1.2.3 The Thyristor

The only member of the thyristor family that we describe in this introduction is the SCR, whose circuit symbol is shown in Fig. 1.2(d). It is a switch that in some ways can be thought of as a "semicontrollable" diode. If no signal is applied to the gate, the device will remain off, independent of the polarity of  $v_{AK}$ . To turn the SCR on, a brief pulse of current,  $i_G$ , is applied to the gate terminal during a time when  $v_{AK} > 0$ . This initiates a regenerative turn-on process that quickly latches the SCR in the on state, in which  $v_{AK} \approx 0$  and the gate no longer has any control over the device. When in this on-state, the SCR can conduct only positive  $i_A$ . It turns off when  $i_A$  tries to go negative. So once on, the SCR behaves as a diode. In summary, the SCR is a diode whose turn-on can be inhibited by not applying a gate pulse.

<sup>†</sup>The use of "K" instead of "C" reflects the Greek origin of the word cathode, or *kathodos*, meaning "way down," that is, the negative terminal.

## 1.3 TRANSFORMERS

Transformers are a prominent feature of power electronic circuits. We treat them extensively in Part III (Chapter 20), but the following introduction to their behavior permits us to use them as circuit elements in Parts I and II.


Transformers are employed to provide electric isolation and the step-up or step-down of ac voltages and currents. The *ideal transformer* shown in Fig. 1.3(a) has two windings of  $N_1$  and  $N_2$  turns. Dots indicate the direction of the windings. If a voltage is applied to one winding so that the dot is positive, the dotted ends of all the other windings (only one in this case) are also positive. If its terminal variables are defined relative to the dots as shown in Fig. 1.3(a), the ideal transformer has the following terminal relationships:

$$\frac{v_1}{v_2} = \frac{N_1}{N_2} \quad (1.1)$$


$$\frac{i_1}{i_2} = -\frac{N_2}{N_1} \quad (1.2)$$

A straightforward application of these relations shows that if an impedance of value  $Z_1$  is connected to terminals 1–1', an impedance of value  $Z_2 = (N_2/N_1)^2 Z_1$  is measured at terminals 2–2'. Using (1.1) and (1.2), we can also show that  $v_1 i_1 = -v_2 i_2$ ; that is, the instantaneous power into one port is equal to the instantaneous power out of the other. The ideal transformer neither dissipates nor stores energy.

A transformer is ideal if it obeys (1.1) and (1.2), but no practical transformer is ideal. In most transformers, the principle departures from ideal result in some voltage and current being "lost" in the transformation, so terminal variables are not precisely related by (1.1) and (1.2). A model that represents these effects is shown in Fig. 1.3(b). Some of the terminal current  $i'_1$  is shunted through the *magnetizing*

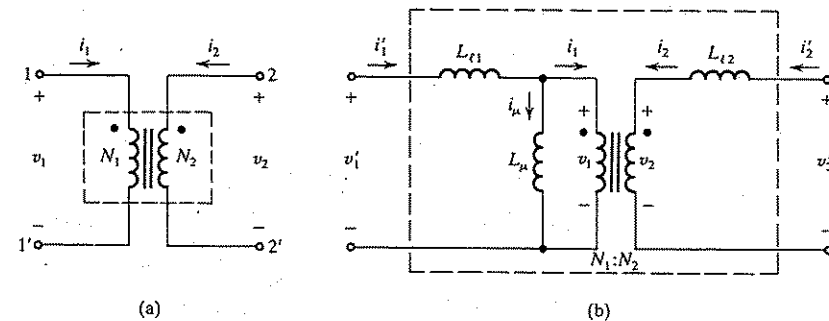

**Figure 1.3** (a) The ideal transformer model. (b) A more practical model, in which the effects of magnetizing inductance ( $L_\mu$ ) and leakage ( $L_{t1}$  and  $L_{t2}$ ) are included.

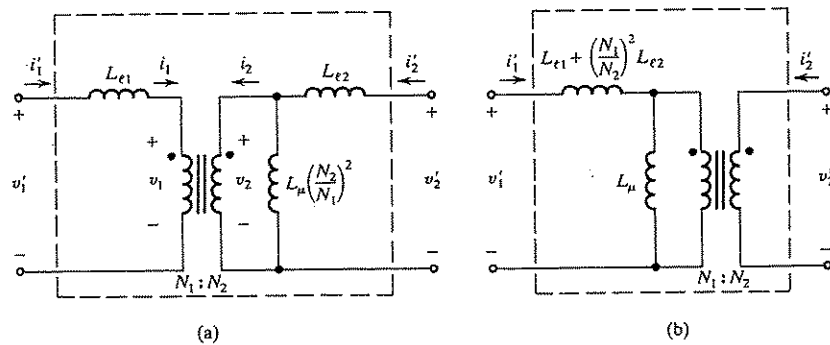

**Figure 1.4** (a) The model of Fig. 1.3(b), with the magnetizing inductance placed on the  $N_2$  side of the ideal transformer. (b) The model of Fig. 1.3(b), simplified by reflecting  $L_{\ell 2}$  through the ideal transformer and combining it with  $L_{\ell 1}$ .

inductance  $L_{\mu}$  and is called the *magnetizing current*. So whereas  $i_1$  and  $i_2$  are still related by (1.1) and (1.2), the real terminal currents  $i'_1$  and  $i'_2$  are not. Similarly, the real terminal voltages  $v'_1$  and  $v'_2$  differ from  $v_1$  and  $v_2$  by the drops across  $L_{\ell 1}$  and  $L_{\ell 2}$ , which are called *leakage inductances*. In Chapter 20 we describe the physical origins of these effects.


Figure 1.3(b) shows  $L_{\mu}$  across the winding  $N_1$ . We can, however, *reflect* it through the ideal transformer so that it appears across the  $N_2$  winding, as shown in Fig. 1.4(a). Sometimes we do this because the result is analytically more convenient to use. Although two leakage inductances, one for each winding, are shown in Fig. 1.3(b), they are often combined by reflecting one through the ideal transformer. If the voltage drop across this inductor is small relative to the voltage across  $L_{\mu}$ , then  $L_{\mu}$  can be moved inside this reflected inductance without introducing much of an error, and the two leakage inductances can be combined. The resulting approximate model is shown in Fig. 1.4(b).

Another useful model transformation is to reflect the entire circuit on one side of the ideal transformer to the other side. A transformation of this kind is shown in Fig. 1.5. There, not only has the magnetizing inductance been reflected to the  $N_1$  side, but the rest of the  $N_2$  side circuit,  $C_o$  and  $R_o$ , has also been “brought through” the ideal transformer. Of course, the isolation function is lost in the transformation, which makes the technique inappropriate for the analysis of some circuits.

We can calculate or measure the leakage and magnetizing inductances of transformers, and we sometimes construct transformers to have specific values for these parameters. And, even though we have been discussing only two winding trans-

formers, similar but somewhat more complicated considerations apply to the modeling of transformers with more than two windings. Other practical considerations, such as the resistance of the windings or losses in the core, are represented by the addition of appropriate elements to the model of Fig. 1.3(b).

Figures 1.3(b) and 1.4 show the schematic transformer representation that we use throughout this book. The circuit model being used to describe a transformer will be enclosed in a dashed box. The model frequently has an ideal transformer as one of its elements, represented by windings with adjacent double bars. Some schematic conventions utilize the double bars to represent an iron core, but we use the bars to indicate the coupled windings of an ideal transformer when it appears inside a dashed box. This convention avoids ambiguity and schematic clutter when more than two windings are involved.

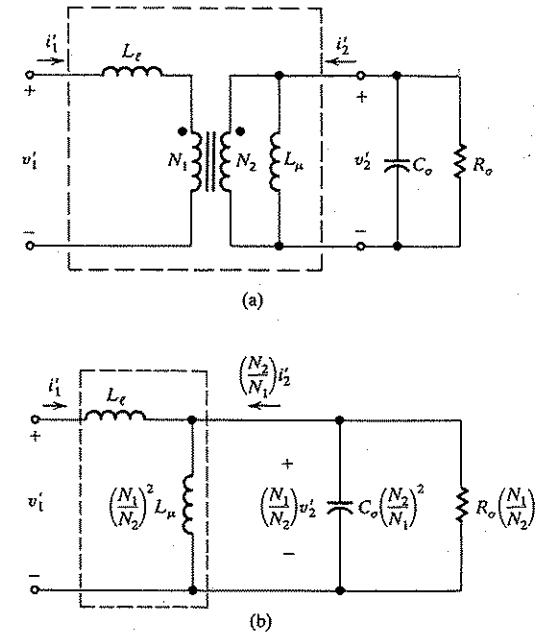

**Figure 1.5** (a) A transformer with an  $RC$  load on the  $N_2$  side. (b) The circuit of (a) with all the  $N_2$  side components reflected to the  $N_1$  side so that the ideal transformer can be eliminated from the transformer model.

## 1.4 NOMENCLATURE

Because we discuss several different kinds of variables, we need to establish their definitions now to avoid confusion later.

1. Variables that may be time dependent are represented by lowercase names, such as  $v_1$ . When necessary for clarification, the time dependence is explicitly indicated, as for example,  $v_1(t)$ .
2. Variables that are constant are represented by uppercase names, such as  $V_1$ ,  $I_{\text{rms}}$ , or  $V_{\text{dc}}$ .
3. The average value or dc component of a periodic variable is denoted by angle brackets around the variable, for example,  $\langle v_o \rangle = V_o$ . Note that the average value is a constant and so is represented by an uppercase name.
4. A *local average* is defined in Chapter 11 and is indicated by an overbar,  $\bar{x}$  or  $\bar{x}(t)$ . Note that the local average is a function of time.
5. Perturbations around a constant value are indicated by a tilde; for instance,  $i_L = I_L + \tilde{i}_L$ .
6. Harmonic components of a nonsinusoidal periodic waveform are indicated by an additional subscript representing the harmonic number. For example,  $v_a = v_{a_1} + v_{a_3} + v_{a_5} + \dots$ .
7. Complex amplitudes of sinusoidal functions are represented by hatted uppercase names:

$$v(t) = V \cos(\omega t + \phi) = \text{Re}(V e^{j\phi} e^{j\omega t}) = \text{Re}(\hat{V} e^{j\omega t})$$

The complex amplitude of  $v(t)$  is  $\hat{V} = V e^{j\phi}$ . The prefix “Re” means “real part of.”

## Notes and Bibliography

We have included an annotated bibliography at the end of most chapters. It provides sources of additional information on topics that you might want to pursue further.

# Form and Function