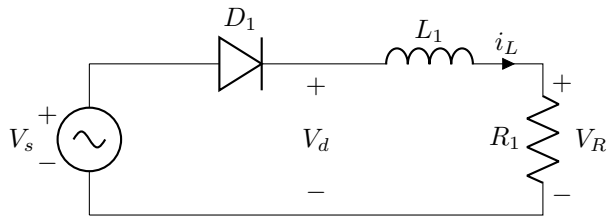


Power Electronics Homework 1

Aidan Sharpe

January 29, 2024

1 Initial Circuit




$$V_s(t) = 110\sqrt{2} \cos(2\pi ft)$$

$$f = 60[\text{Hz}]$$

$$L_1 = 20[\text{mH}]$$

$$R_1 = 10[\Omega]$$

2 Diode is "On"

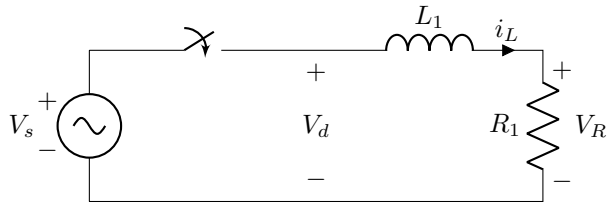

$$V_d(t) = V_s(t) = V_L(t) + V_R(t)$$

$$V_L(t) = L_1 \frac{d}{dt} i_L(t)$$

$$V_R(t) = R_1 i_L(t)$$

$$110\sqrt{2} \cos(120\pi t) = 10i_L(t) + 0.02 \frac{d}{dt} i_L(t)$$

Apply Laplace Transform:

$$10I_L(s) + 0.02sI_L(s) + i_L(0) = \frac{110\sqrt{2}s}{14400\pi^2 + s^2}$$

Solve for $I_L(s)$:

$$I_L(s)(10 + 0.02s) = \frac{110\sqrt{2}s}{14400\pi^2 + s^2}$$


$$I_L(s) = \frac{110\sqrt{2}s}{\left(\frac{s}{50} + 10\right)(s^2 + 14400\pi^2)}$$

Apply Inverse Laplace Transform:


$$i_L(t) = \frac{6875\sqrt{2}\cos(120\pi t) + 1650\pi\sqrt{2}\sin(120\pi t)}{36\pi^2 + 625} - \frac{6875\sqrt{2}e^{-500t}}{36\pi^2 + 625}$$

$$V_R = \frac{10(6875\sqrt{2}\cos(120\pi t) + 1650\pi\sqrt{2}\sin(120\pi t))}{36\pi^2 + 625} - \frac{68750\sqrt{2}e^{-500t}}{36\pi^2 + 625}$$

3 Diode Is "Off"

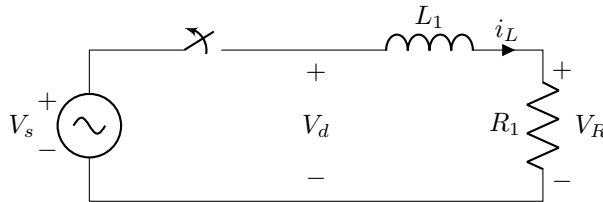

4 LTSpice

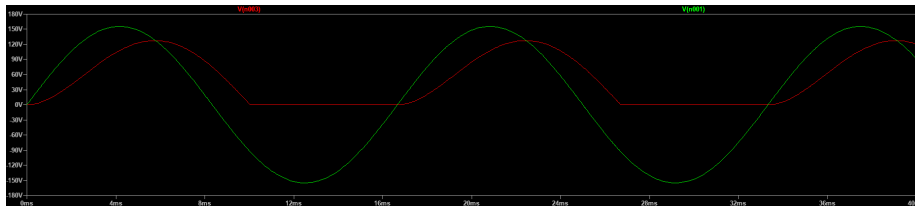

5 MATLAB

```
syms s t
R_1 = 10;
L_1 = 0.02;
```

```
v_s = 110*sqrt(2)*cos(120*pi*t);
```

```
V_s = laplace(v_s);
```

```
I_L = V_s / (R_1 + s*L_1);
```

```
i_L = ilaplace(I_L);
```

```
v_o = i_L * R_1
```

6 Large Inductor

As the inductor gets proportionally larger than the resistor, the amplitude of the output voltage decreases and the phase shift increases.

7 Large Resistor

As the resistor gets proportionally larger than the inductor, the amplitude of the output approaches the amplitude of the input and the phase shift goes to zero.