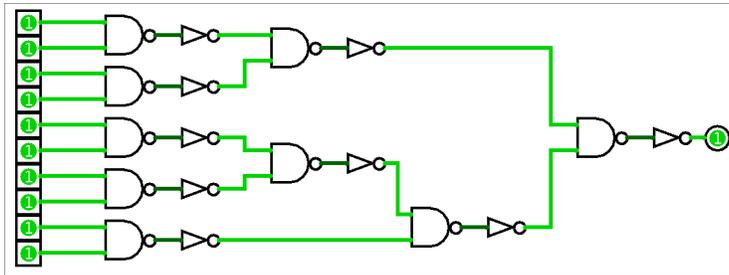


VLSI Homework 12 - Aidan Sharpe

Problem 12.5

Estimate the minimum delay of a 10:1024 decoder driving an electrical effort of $H = 20$.

A 10:1024 decoder will contain 1024 AND gates. It will have a branching effort of $B = 1024/2 = 512$. Assuming $G \approx 1$ for a 10-input AND gate, the path effort will be $F = GBH = 40960$. The optimal number of stages will be, assuming the stage effort is $\rho = 4$, $\hat{N} = \log_4(40960) = 7.66$. We will use 8 stages in our solution, seen below.



Using static CMOS gates

For a static CMOS design, $G = (4/3)^4 = 256/81$. Therefore, the actual stage effort is $F = GBH = 32363.5$. The parasitic delay is $P = 12$, so the total delay will be $D = NF^{1/N} + P = 41.3\tau$.

Using footless domino gates

A footless domino design has $g = 1/3$ for inverters and $g = 2/3$ for NAND2. Therefore, $G = (1/3)^4(2/3)^4 = 16/6561$, and $F = GBH = 24.97$. The parasitic delay for inverters is $p = 2/3$, and $p = 1$ for NAND2. Therefore, the path parasitic delay is $P = 4 + 8/3 = 20/3$. Finally, the total delay will be $D = NF^{1/n} + P = 18.62\tau$.

Problem 12.12

NAND ROMs will have a higher resistance than a comparable NOR ROM, thereby making them slower.